

Explore ~

Q (/local/search/page/)

Login (/site/login/?next=/p/6738/design-mealy-sequence-detector-to-detect-a-seque-1/)

Design mealy sequence detector to detect a sequence ---- using D filpflop and logic





written 4.3 years ago by • modified 4.3 years ago





Mumbai University > ELECTRO > Sem 3 > Digital Circuits and Designs

Marks: 10M

Year: Dec 2014

mumbai university (/t/mumbai university/) digital circuits and design (/t/digital circuits and design/) • 51k views



ADD COMMENT



written 4.3 years ago by



• A sequence detector is a sequential state machine. In a Mealy machine, output depends on the present state and the external input (x). Hence in the diagram, the output is written outside the states, along with inputs. The state diagram of a Mealy machine for a 1010 detector is:

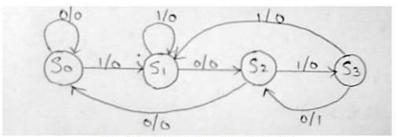


Fig14. State diagram for 1010 detector

• The state table for the above diagram:

Present state	Next	state	Output		
	X=0	× =1	×=0	×=1	
50	50	Si	0	0	
SI	52	SI	0	0	
S ₂	So	53	0	0	
53	52	Sı	11	1	

Fig15. State table for above state diagram

• State assignments: Let S_0 = 00

 S_1 = 01

 S_2 = 10

 S_3 = 11

The above state table becomes:

Present State	Next	state	Output		
	X=0	X=1	X=0	X=1	
00	00	01	0	0	
01	10	01	0	0	
10	00	11	0	0	
1.1	10	1.1	1	0	

Fig16. State table with state assignments

- Four states will require two flip flops. Consider two D flip flops. Their excitation table is shown below.
- Excitation table:

Bresent State		Input	Next State		F/F Inputs		Outpo
		×			DE		
0	0	0	0	0	112 10 00000	0	
0	0	1	0	1	0	1	0
-0	1	0	1	0	1	0	0
0	11	1	0	1	0	1	0
1	0	0	0	0	0	0	0
1	0	1	1	1	1	1	0
1	1	0	1	0	1	0	1
1	1	1	1	1	1	1	0

Fig17. Excitation table

• K-maps to determine inputs to D Flip flop:


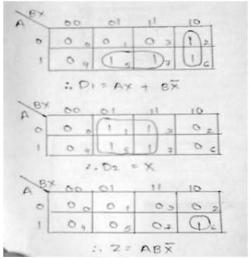


Fig. K-maps

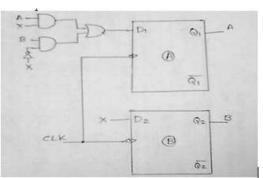• Circuit diagram for the sequence detector:






ADD COMMENT

if i design it using 5 states, is the method wrong in case of mealy FSM?

ADD REPLY

written 2.9 years ago by

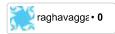

Please log in (/site/login/?next=/p/6738/design-mealy-sequence-detector-to-detect-a-seque-1/) to add an answer.

Continue reading

Find answer to specific questions by searching them here. It's the best way to discover useful content.

Find more (/local/search/page/)





(market://details?

id=com.ques10&utm_source=global_co&utm_medium=prtnr&utm_content=Mar2515&utm_campaign=PartBadge&pcampaignid=MKT-Other-global-all-co-prtnr-py-PartBadge-Mar2515-1)

Engineering in your pocket

Download our mobile app and study on-the-go. You'll get subjects, question papers, their solution, syllabus - All in one app.

COMPANY

About Us (/info/about/) Community (/user/list/) Blog (/t/blog)

CONTENT

New Post (/p/new/post/)
All Posts (/t/latest/)
Badges (/b/list/)

SUPPORT

Contact Us (/info/contact/)
Privacy (/info/privacy/)
Terms (/info/terms/)



https://www.youtube.com/playlist?list=UUH-lr-oL_apReZzPeFGJopg)



(https://in.linkedin.com/company/ques10)

ftel:+919503733731)

(https://wa.me/919503733731)